



Vivekanand Education Society's Institute of Technology
An Autonomous Institute Affiliated to University of Mumbai

**End Semester Examination
Summer 2024**

Max marks: 60

Duration: 2 hours

Branch: Automation & Robotics

Semester: IV

Name of the Course: Signal Conditioning Circuit Design

Course code: ARC404

QP Code: R23-ARC404_012023-24

- N.B.** (1) Attempt any three out of the five questions.
(2) Figures to the right indicate full marks.
(3) Assume suitable data if necessary

Marks

- | | | |
|---------|---|----|
| Q.1 (a) | Explain with a block diagram, the working of data acquisition system. | 10 |
| (b) | Derive and explain the gain of inverting and non-inverting amplifier. Determine the value of R_f of a non-inverting amplifier with gain 15 and input resistance (R_i) of 2 k Ω . | 10 |
| Q.2 (a) | Explain the concept of loading and use of op-amp to avoid the same, with suitable example. | 10 |
| (b) | Explain the working of V-to-F converter, with suitable diagram. | 10 |
| Q.3 (a) | Sketch the circuit diagram of an ideal differentiator. Explain the limitations of it and show how it can be modified into a practical differentiator. | 10 |
| (b) | Explain the working of flash type ADC, with circuit diagram. | 10 |
| Q.4 (a) | Design the circuit of an Astable Multi-vibrator using IC555 for 90% duty cycle. | 10 |
| (b) | Explain the linear application of op-amp as:
i. Subtractor
ii. Current-to-Voltage converter | 10 |
| Q.5 (a) | Explain the working of RC phase shift oscillator, with diagram. Also design a RC phase shift oscillator that oscillates at 5 kHz. | 10 |
| (b) | Explain the signal conditioning circuit for optical sensors in detail. | 10 |

X-----X-----X-----X

QP Code: R23-ARC404_012023-24